

DIGITAL ELECTRONIC CIRCUITS LAB


EXPERIMENT 2

Utkarsh Patel (18EC30048)

Objective

To display the 8 characters of roll number one after another using 7447 IC, 7493 IC, 7-segment display and logic gates.

Circuit Diagram

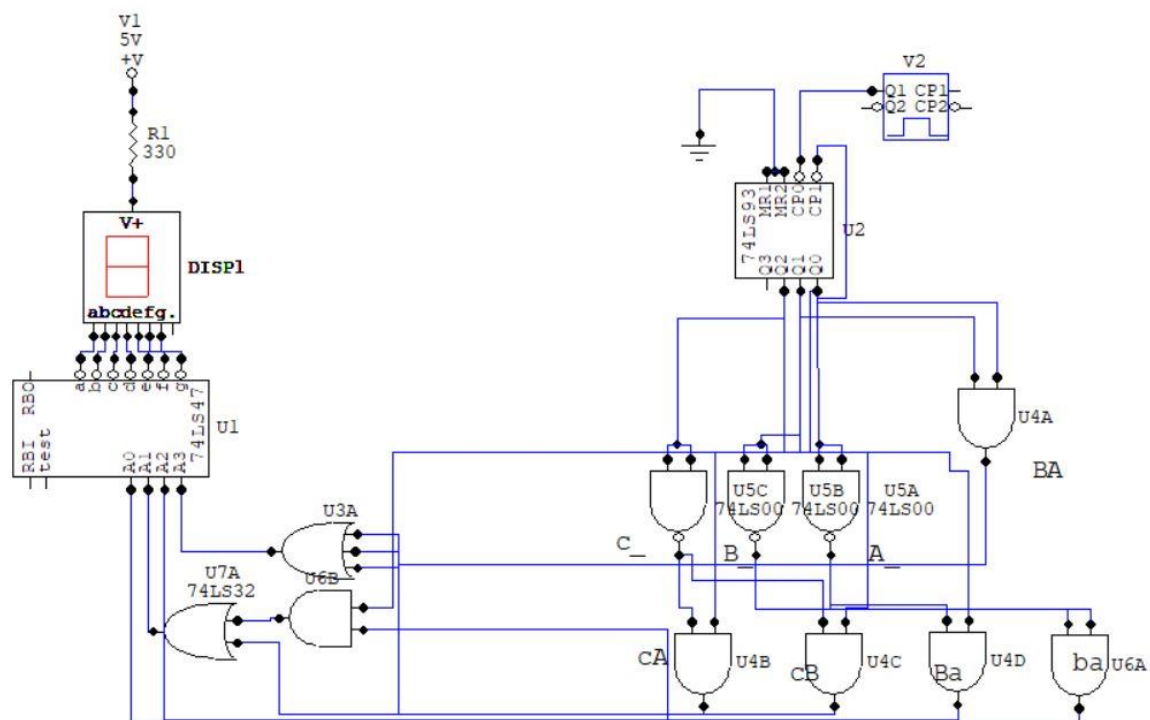

Truth Table

In this experiment, $\langle C, B, A \rangle$ denotes the bits obtained from 7493 IC excluding the MSB. It is then mapped to $\langle Z, W, Y, X \rangle$ to represent the characters using logic gates.

m	C	B	A	Z	W	Y	X
0	0	0	0	0	0	0	1
1	0	0	1	1	0	0	0
2	0	1	0	1	1	1	0
3	0	1	1	1	0	1	0
4	1	0	0	0	0	1	1
5	1	0	1	0	0	0	0
6	1	1	0	0	1	0	0
7	1	1	1	1	0	0	0

K-maps

- $Z = AB + \bar{C}B + \bar{C}A$

		BA			
		00	01	11	10
C	0		1	1	1
	1			1	

- $W = B\bar{A}$

		BA			
		00	01	11	10
C	0				1
	1				1

- $Y = C\bar{B}\bar{A} + \bar{C}B$

		BA			
		00	01	11	10
C	0			1	1
	1	1			

- $X = \bar{B}\bar{A}$

		BA			
		00	01	11	10
C	0	1			
	1	1			

Results

During simulation, the circuit was observed to display the 8 characters of my roll number, i.e. **18EC3048** in a loop. The link for the simulation is given below.

https://drive.google.com/file/d/1q1_Y2Qxg5XZYKj0tljUsn2K595wZonjI/view?usp=sharing

Discussion:

- In this experiment, I simulated the circuit to display the eight characters of my roll number using a 7-segment display, a 7447 IC, a 7493 IC, a clock and few logic gates.
- A potential difference of about 1.6 V is required to light up a red LED.
- Calculating value of resistance R in the circuit:
 - The current in the circuit is bounded by 10 mA. The voltage supply was fixed to 5 V. Therefore, $R = \frac{5-1.6}{10} \frac{V}{mA} = 330 \text{ ohms}$
- The input of the 7-segment display is controlled using 7447 and 7493 IC.
 - 7493 IC converts a digit to into its binary representation.
 - 7447 IC is provided with this binary representation, and it maps it to the sequence needed to display a particular digit in 7-segment display.
- A clock is provided as input to 7493 IC of least significant digit. The falling edge of the clock is employed as trigger for the IC.
- In order to map the characters with the counter, truth table was constructed.
- The mapping was further simplified using K-maps. In this experiment, $\langle C, B, A \rangle$ denotes the bits obtained from 7493 IC excluding the MSB. It is then mapped to $\langle Z, W, Y, X \rangle$ to represent the characters.

